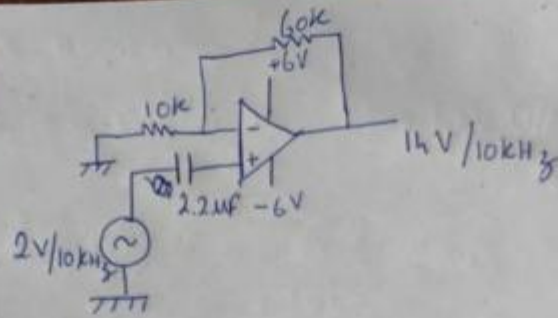


## Q2 PARTA



Gain

$$A_v = 1 + \frac{R_f}{R_i} = 7$$

$$\frac{R_f}{R_i} = 6$$

Let's assume  $R_i = 10k$   
and  $R_f = 60k$

→ Since the input signal is an AC sine wave, use a coupling capacitor  $C_{in}$  to block DC component.

$$f_c = \frac{1}{2\pi R_i C_{in}} \Rightarrow C_{in} = \frac{1}{2\pi R_i f_c} = \frac{1}{2\pi \times 10^4 \times 10^4}$$

$$\text{Considering } f_c = 10\text{Hz} \quad = 1.59 \mu\text{F}$$

$$\text{OR } 1.6 \mu\text{F}$$

A standard 2.2 uF capacitor can be used.