

classmate
Date _____
Page _____

The goal is to step down 5V to 2.5V with an output current of 0.1A, while maintaining a 2% output ripple voltage. The design also ensures galvanic isolation between input and output allowing for both step-up and step-down operations.

1) Coupled Inductor or Transformer :-

A transformer was chosen for this design due to its ability to provide full galvanic isolation, ensuring electrical protection between input and output. Coupled inductors lack complete isolation and are better suited for non-isolated topologies.

2) Step down and Step up functionality

The topology used is a flyback converter, which inherently supports both step-down and step-up operations.

The transformer's turn ratio determines whether the output is stepped up or down.

3) Given specification :-

⇒ Input voltage (V_{in}) = 5V

Output voltage (V_{out}) = 2.5V

Output current (I_{out}) = 0.1A

Ripple voltage (Ripple V_{out}): 2% of V_{out} = 0.05V

Switching frequency (assume) = 100 kHz

Assume it is working in DCM (Discontinuous Conduction Mode).

a) Turns ratio (n)

$$n = \frac{V_{out} + V_{diode}}{V_{in} \times D}$$

$$m = \frac{2.5 + 0.7}{(5 \times 0.5)} = 1.28 \quad \text{and } V_{\text{diode}} = 0.7V$$

Chosen $m = 1.3$

b) Primary inductance (L_m)

$$L_m \geq \frac{V_m \times D}{\Delta I_L \times f_s}$$

$$\Delta I_L = 0.3 \times I_{\text{out}} = 0.03A$$

generally peak to peak ripple current (ΔI_L) is typically 20% - 40% of output current, we take assume 30%.

$$L_m = \frac{5 \times 0.5}{(0.03 \times 100 \text{ kHz})} = 833 \mu H$$


Chosen $L_m = 1 \text{ mH}$

c) Output capacitor (C_{out}): The output capacitor filters the ripple voltage.

$$C_{\text{out}} = \frac{\Delta I_L}{86.5 V_{\text{out}}}$$

$$C_{\text{out}} = \frac{0.03}{8.100 \times 10^3 \times 0.05} = 7.5 \mu F$$

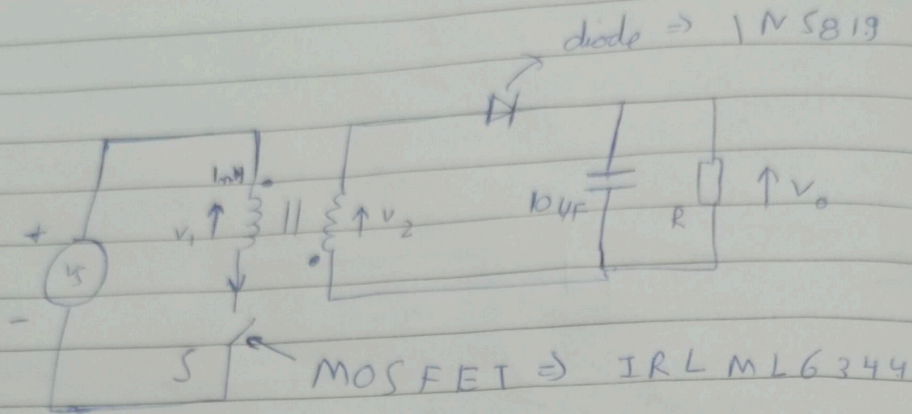Choose a standard capacitor value $C_{\text{out}} = 10 \mu F$
IRLML6344 Mosfet and 1N5819 diode.



turn ratio = 1.3

flyback converter